

Computer Organization

RTL Design

Ilkwon Byun

High Performance Computer System (HPCS) Lab

April 01, 2018

Objective


- To review register transfer level (RTL) designs

Previous Labs

- Lab 01: Introduction to Verilog (1)
 - Modeling combinational circuits in Verilog
 - Implementing a 16-bit ALU
- Lab 02: Sequential Logic & RTL
 - Modeling a simple FSM (010 detector)
 - Simple register file with read/write
- Now we are ready to implement a more complicated FSM (vending machine)

RTL design (review)


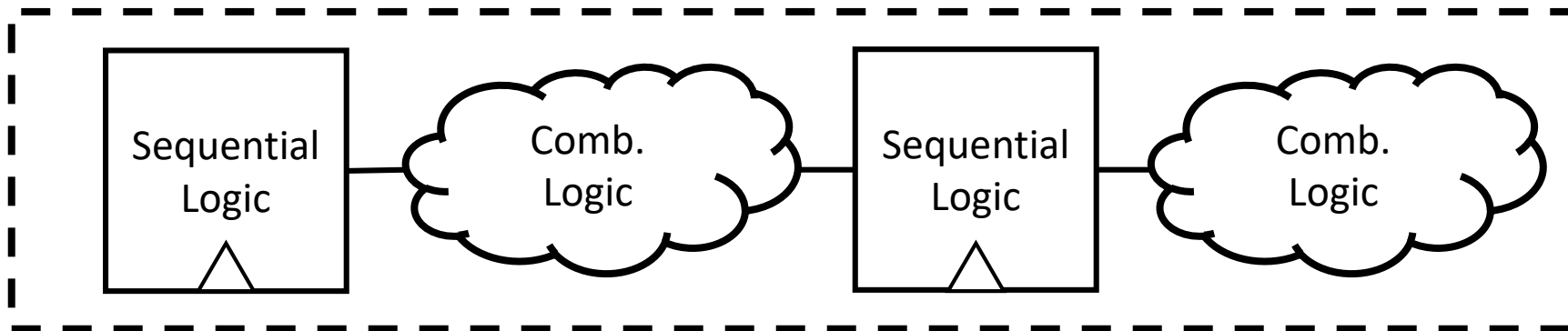
- Design logic to implement synchronous circuit
 - Dataflow between registers (Sequential Logic)
 - Logical operation with register values (Combinational Logic)



RTL design (review)


- Understand what should be stored in each clock signal
 - Ex) **Current state** of FSMs
- How stored data should be updated
 - Ex) **Current state** -> **Next state**
- Find out and understand combinational logic for stored data and output
 - Ex) **Next state** and **Output** of FSMs

RTL design (review)

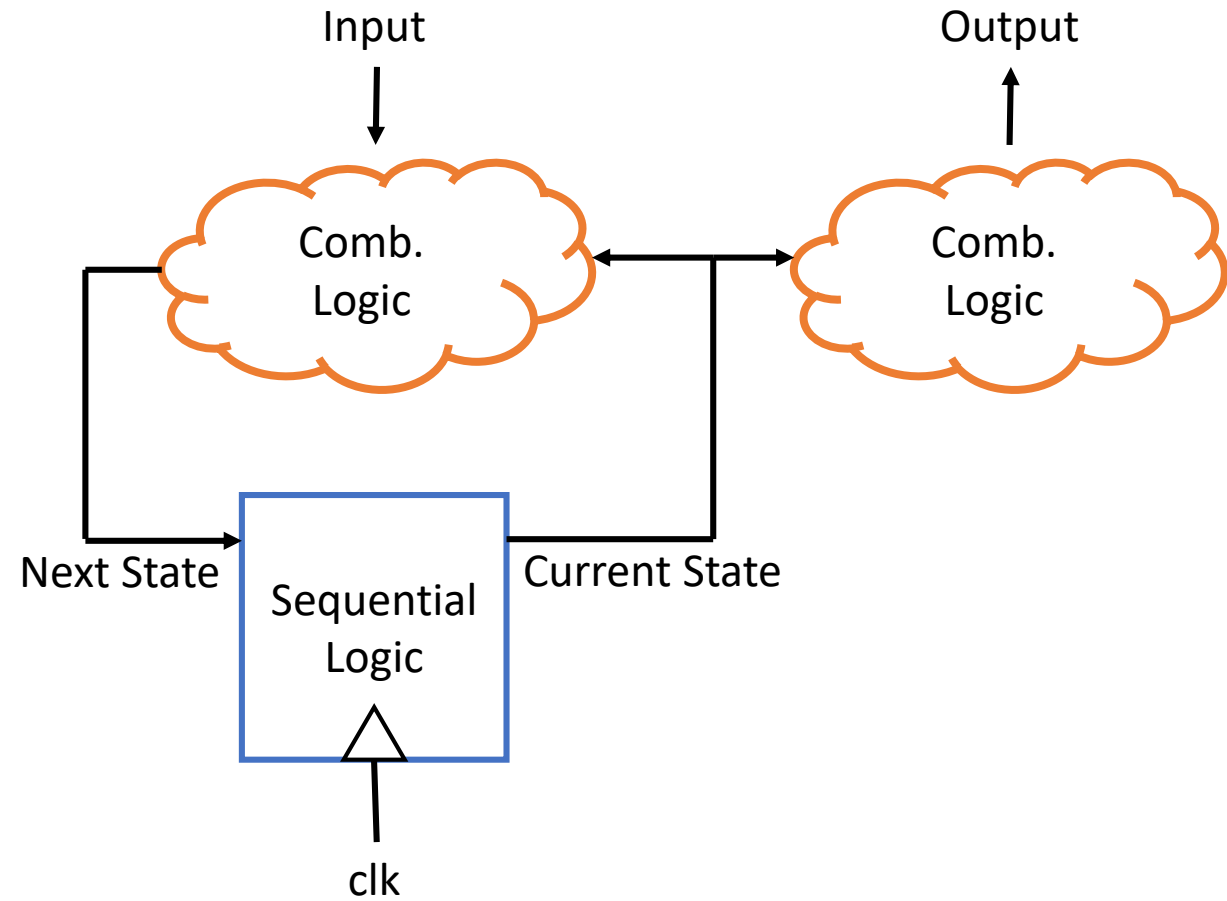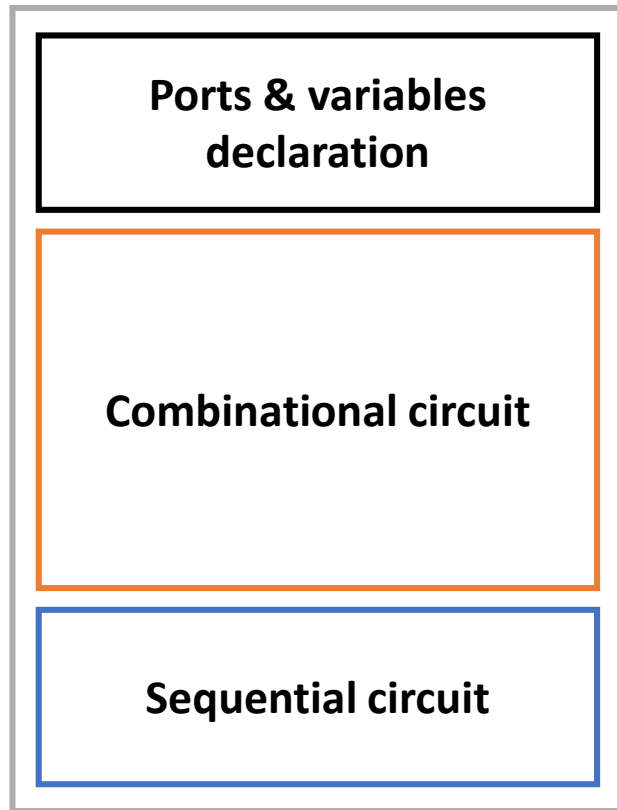

Assignment #3: Vending Machine

Assign #3: Vending Machine

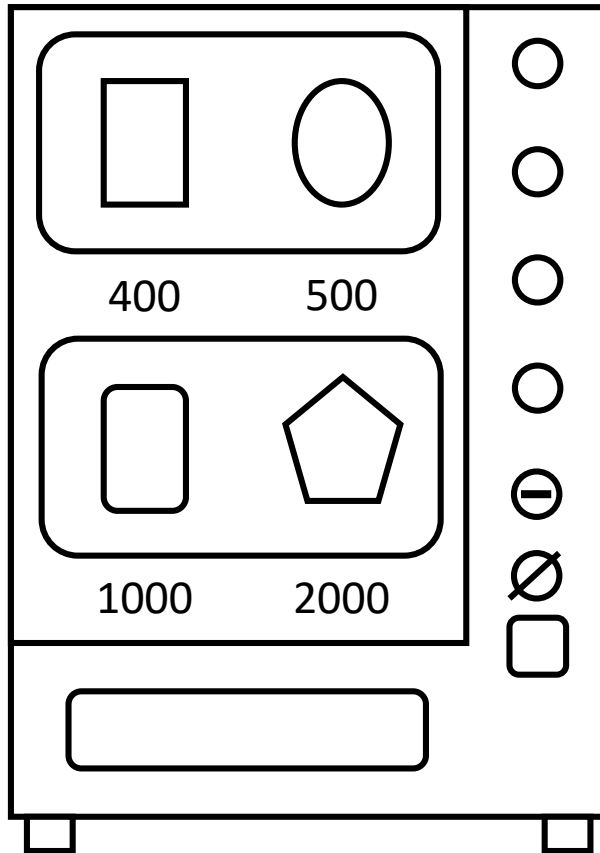

- There is a vending machine with **4 items** in it
 - Price: 400, 500, 1000, 2000
- It receives **3 types of coins** (100, 500, 1000)
- There is a **return button**
 - When triggered, the machine returns change

Assign #3: Vending Machine Functionality

- When a user inserts a coin
 - **Available** item is shown
- When a user selects an item
 - If the selected item is available -> item is sold
 - If the selected item is not available -> nothing happens
 - Assume **infinite amount** of items
- When a user presses return button
 - The total **number of coins** for the change is returned (with the least amount)
 - Ex) When the change is 1700 -> it is returned with $1000*1$, $500*1$ and $100*2$
 - Assume **infinite amount** of coins

Assign #3: Vending Machine Ports

- Implement a simple vending machine with 4 items and 3 types of coins (**do not modify port name of the skeleton code!!** Otherwise, you will get **0 point** for this lab)
 - Input
 - i_input_coin: 3bit input (if x^{th} bit is set to 1, x^{th} coin is inserted)
 - i_select_item: 4bit input (if x^{th} bit is set to 1, x^{th} item is selected)
 - i_trigger_return: trigger return button of the vending machine
 - Output
 - o_available_item: 4bit output (shows availability of each item, 1 if x^{th} item is not out of stock && current change \geq price of the item)
 - o_output_item: 4bit output (if x^{th} item is sold, x^{th} bit is set to 1)
 - o_return_coin: the number of coin returned (**only if the machine has enough change**) when received i_trigger_return
 - o_current_total: the sum of money a user has inserted and used up (total amount of change)